

# 第三章 时序电路的分析与设计

## 学习要求：

### 3.1 时序逻辑电路

- 熟悉时序电路的一般形式、分类和描述方法
- 掌握时序电路双稳态元件的内部结构、逻辑符号、次态真值表和次态方程

### 3.2 熟练掌握同步时序逻辑电路的分析和设计方法

### 3.3 掌握脉冲异步时序逻辑电路的分析和设计方法\*

### 3.4 熟练掌握常用时序中规模集成电路MSI和555定时电路的应用

## 3.2 同步时序电路的分析与设计

### 1. 同步时序电路的分析

- 同步时序电路分析的一般步骤
- 同步时序电路分析举例


### 2. 同步时序电路的设计

- 同步时序电路设计步骤
- 建立原始状态图和原始状态表——构图法
- 状态化简：完全给定与不完全给定同步时序电路状态表的化简
- 状态分配：相邻状态分配法
- 激励函数和输出函数的确定
- 电路分析与说明、设计举例

### 3.2.3 设计举例

**例1** 设计一个“1111”序列检测器。当连续收到四个(或四个以上)“1”后，电路输出  $Z=1$ ；否则，输出  $Z=0$ 。(书例3-9对应D触发器实现)

① 画出原始状态图

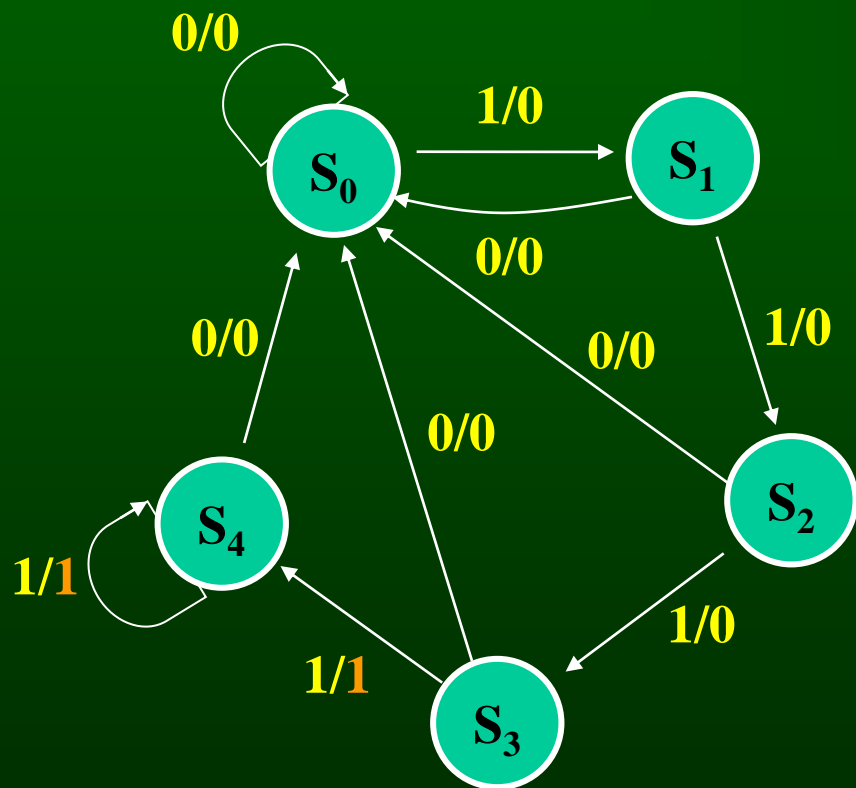

② 写出原始状态表

$y \backslash x$	0	1
$S_0$	$S_0/0$	$S_1/0$
$S_1$	$S_0/0$	$S_2/0$
$S_2$	$S_0/0$	$S_3/0$
$S_3$	$S_0/0$	$S_4/1$
$S_4$	$S_0/0$	$S_4/1$

### ③ 隐含表

$S_1$	$S_1 \times S_2$			
$S_2$	$S_1 \times S_3$	$S_2 \times S_3$		
$S_3$	$\times$	$\times$	$\times$	
$S_4$	$\times$	$\times$	$\times$	$\checkmark$
	$S_0$	$S_1$	$S_2$	$S_3$

### 原始状态表

$y \backslash x$	0	1
$S_0$	$S_0/0$	$S_1/0$
$S_1$	$S_0/0$	$S_2/0$
$S_2$	$S_0/0$	$S_3/0$
$S_3$	$S_0/0$	$S_4/1$
$S_4$	$S_0/0$	$S_4/1$

### ④ 最大等效类及命名

$S_0$	$S_1$	$S_2$	$(S_3, S_4)$
$\downarrow$	$\downarrow$	$\downarrow$	$\downarrow$
A	B	C	D

### ⑤ 最小化状态表

$y \backslash x$	0	1
A	A/0	B/0
B	A/0	C/0
C	A/0	D/0
D	A/0	D/1

## ⑥ 状态分配(1)

分配方案之一:

$$R_{CD} = 1$$

$$m_{AB} = 1, m_{AC} = 1, m_{AD} = 2$$

$$l_{AB} = 1, l_{AC} = 1, l_{BC} = 1$$

$y_0 \backslash y_1$	0	1
0	A	C
1	B	D

$$E_{AB} = 2R_{AB} + m_{AB} + 2l_{AB} = 3$$

$$E_{AC} = 2R_{AC} + m_{AC} + 2l_{AC} = 3$$

$$E_{AD} = 2R_{AD} + m_{AD} + 2l_{AD} = 2$$

$$E_{BC} = 2R_{BC} + m_{BC} + 2l_{BC} = 2$$

$$E_{CD} = 2R_{CD} + m_{CD} + 2l_{CD} = 2$$

最小化状态表

$y \backslash x$	0	1
A	A/0	B/0
B	A/0	C/0
C	A/0	D/0
D	A/0	D/1

## 状态分配(2)

分配方案之二:

$$R_{CD} = 1$$

$$m_{AB} = 1, m_{AC} = 1, m_{AD} = 2$$

(可忽略  $l_{AB} = 1, l_{AC} = 1, l_{BC} = 1$ )

$y_0 \backslash y_1$	0	1
0	A	D
1	B	C

## 最小化状态表

$$E_{AB} = 2R_{AB} + m_{AB} + 2l_{AB} = 1$$

$$E_{AC} = 2R_{AC} + m_{AC} + 2l_{AC} = 1$$

$$E_{AD} = 2R_{AD} + m_{AD} + 2l_{AD} = 2$$

$$E_{CD} = 2R_{CD} + m_{CD} + 2l_{CD} = 2$$

$y \backslash x$	0	1
A	A/0	B/0
B	A/0	C/0
C	A/0	D/0
D	A/0	D/ <b>1</b>

## 7、求激励函数和输出函数的表达式

$y_1y_0 \backslash x$		0	1
A	00	00/0	01/0
B	01	00/0	11/0
C	11	00/0	10/0
D	10	00/0	10/1

二进制状态表

$$D_1 = x \cdot y_1 + x \cdot y_0$$

$$D_0 = x \cdot \bar{y}_1$$

$$Z = x \cdot y_1 \cdot \bar{y}_0$$

Q	$Q^{n+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

激励表

$y_1y_0 \backslash x$	0	1
00	0	0
01	0	1
11	0	1
10	0	1

$D_1$


$y_1y_0 \backslash x$	0	1
00	0	1
01	0	1
11	0	0
10	0	0

$D_0$

$y_1y_0 \backslash x$	0	1
00	0	0
01	0	0
11	0	0
10	0	1

Z

## “1111”序列检测器逻辑电路图

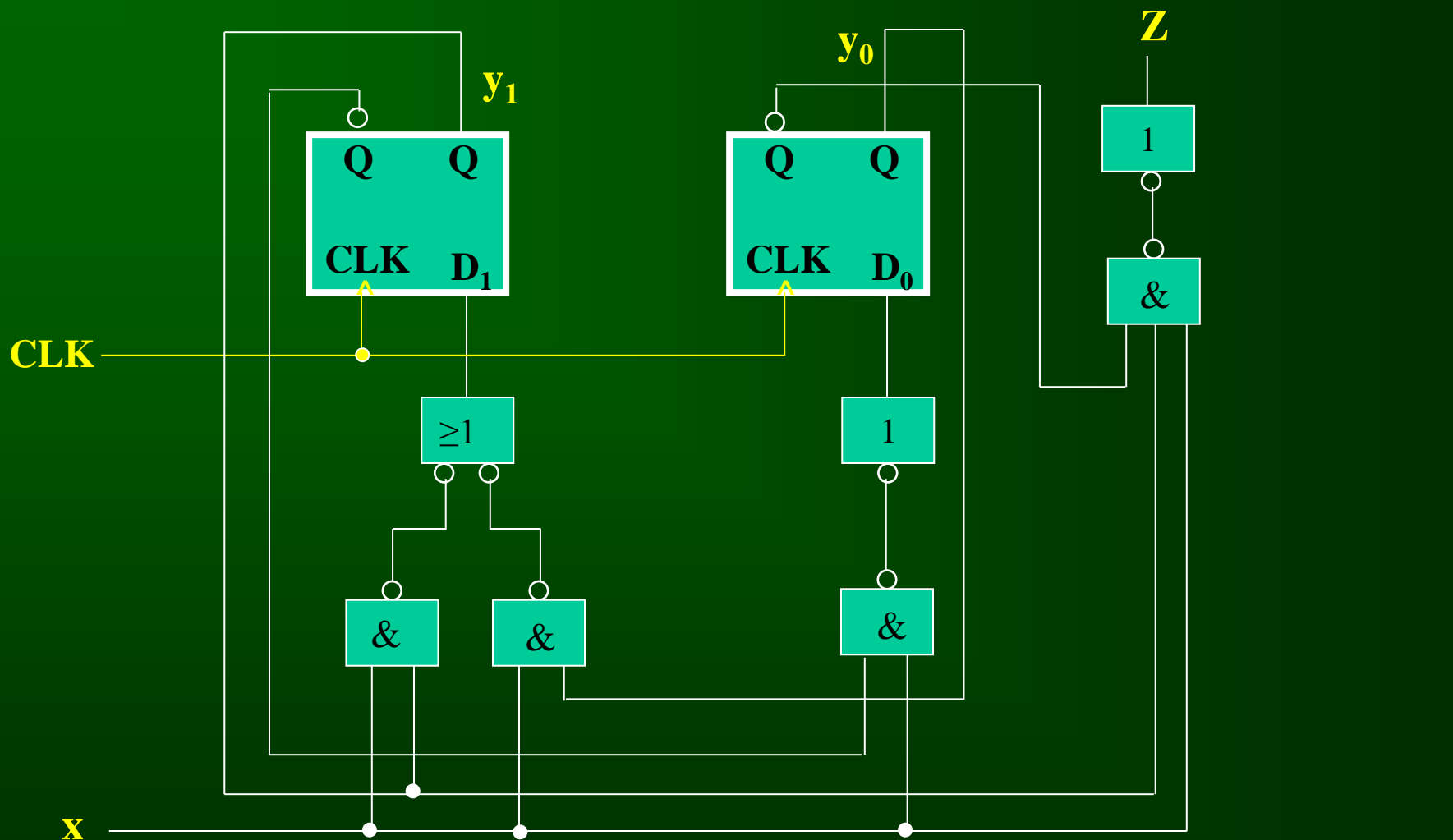

$$D_1 = x \cdot y_1 + x \cdot y_0$$

$$D_0 = x \cdot \bar{y}_1$$

$$Z = x \cdot y_1 \cdot \bar{y}_0$$

因为卡诺图中没有无关项d出现，因此不会出现挂起现象。



**例2** 用JK触发器设计一个**六进制可逆计数器**。当  $x=1$  时，加1计数；当  $x=0$  时，减1计数。

分别用二进制 000~101 表示六进制中的 6 个状态。

$y_2y_1y_0 \backslash x$	0	1
000	101	001
001	000	010
010	001	011
011	010	100
100	011	101
101	100	000
110	ddd	ddd
111	ddd	ddd

$y_1y_0 \backslash xy_2$	01	11
11	d	d
10	d	d

**例2** 用JK触发器设计一个六进制可逆计数器。当  $x=1$  时，加1计数；当  $x=0$  时，减1计数。

分别用二进制 000~101 表示六进制中的 6 个状态。

$y_2y_1y_0 \backslash x$	0	1
000	101	001
001	000	010
010	001	011
011	010	100
100	011	101
101	100	000

$y_1y_0 \backslash xy_2$	0	1
00		
01		
10	d	d
11	d	d

$J_2$

$y_1y_0 \backslash xy_2$	0	1
00		
01		
10	d	d
11	d	d

$J_1$

$y_1y_0 \backslash xy_2$	0	1
00		
01		
10	d	d
11	d	d

$J_0$

$y_1y_0 \backslash xy_2$	0	1
00		
01		
10	d	d
11	d	d

$K_2$

$y_1y_0 \backslash xy_2$	0	1
00		
01		
10	d	d
11	d	d

$K_1$

$y_1y_0 \backslash xy_2$	0	1
00		
01		
10	d	d
11	d	d

$K_0$

二进制状态表

Q	$Q^{n+1}$	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

激励表

**例2** 用JK触发器设计一个六进制可逆计数器。当  $x=1$  时，加1计数；当  $x=0$  时，减1计数。

分别用二进制 000~101 表示六进制中的 6 个状态。

$y_2y_1y_0 \backslash x$	0	1
000	101	001
001	000	010
010	001	011
011	010	100
100	011	101
101	100	000

$y_1y_0 \backslash xy_2$	1	d	d	0
1	1	d	d	0
0	0	d	d	0
0	0	d	d	1
0	0	d	d	0

$J_2$

$y_1y_0 \backslash xy_2$				
1				
0				
0		d	d	
0		d	d	

$J_1$

$y_1y_0 \backslash xy_2$				
1				
0				
0		d	d	
0		d	d	

$J_0$

$y_1y_0 \backslash xy_2$	d	1	0	d
1	d	1	0	d
0	d	0	1	d
0	d	d	d	d
0	d	d	d	d

$K_2$

$y_1y_0 \backslash xy_2$				
1				
0				
0		d	d	
0		d	d	

$K_1$

$y_1y_0 \backslash xy_2$				
1				
0				
0		d	d	
0		d	d	

$K_0$

二进制状态表

Q	$Q^{n+1}$	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

激励表

**例2** 用JK触发器设计一个六进制可逆计数器。当  $x=1$  时，加1计数；当  $x=0$  时，减1计数。

分别用二进制 000~101 表示六进制中的 6 个状态。

$y_2y_1y_0 \backslash x$	0	1
000	101	001
001	000	010
010	001	011
011	010	100
100	011	101
101	100	000

$y_1y_0 \backslash xy_2$	1	d	d	0
01	1	d	d	0
00	0	d	d	0
11	0	d	d	1
10	0	d	d	0

$J_2$

$y_1y_0 \backslash xy_2$	0	1	0	0
01	0	1	0	0
00	0	0	0	1
11	d	d	d	d
10	d	d	d	d

$J_1$

$y_1y_0 \backslash xy_2$				
01				
00				
11		d	d	
10		d	d	

$J_0$

$y_1y_0 \backslash xy_2$	d	1	0	d
01	d	1	0	d
00	d	0	1	d
11	d	d	d	d
10	d	d	d	d

$K_2$

$y_1y_0 \backslash xy_2$	d	d	d	d
01	d	d	d	d
00	d	d	d	d
11	0	d	d	1
10	1	d	d	0

$K_1$

$y_1y_0 \backslash xy_2$				
01				
00				
11		d	d	
10		d	d	

$K_0$

二进制状态表

Q	$Q^{n+1}$	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

激励表

**例2** 用JK触发器设计一个六进制可逆计数器。当  $x=1$  时，加1计数；当  $x=0$  时，减1计数。

分别用二进制 000~101 表示六进制中的 6 个状态。

$y_2y_1y_0 \backslash x$	0	1
000	101	001
001	000	010
010	001	011
011	010	100
100	011	101
101	100	000

$y_1y_0 \backslash xy_2$	1	d	d	0
01	1	d	d	0
00	0	d	d	0
11	0	d	d	1
10	0	d	d	0

$J_2$

$y_1y_0 \backslash xy_2$	0	1	0	0
01	0	1	0	0
00	0	0	0	1
11	d	d	d	d
10	d	d	d	d

$J_1$

$y_1y_0 \backslash xy_2$	1	1	1	1
01	1	1	1	1
00	d	d	d	d
11	d	d	d	d
10	1	d	d	1

$J_0$

$y_1y_0 \backslash xy_2$	d	1	0	d
01	d	1	0	d
00	d	0	1	d
11	d	d	d	d
10	d	d	d	d

$K_2$

$y_1y_0 \backslash xy_2$	d	d	d	d
01	d	d	d	d
00	d	d	d	d
11	0	d	d	1
10	1	d	d	0

$K_1$

$y_1y_0 \backslash xy_2$	d	d	d	d
01	d	d	d	d
00	1	1	1	1
11	1	d	d	1
10	d	d	d	d

$K_0$

二进制状态表

Q	Q <sup>n+1</sup>	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

激励表

# 激励函数表达式

$$J_2 = x \cdot y_1 \cdot y_0 + \bar{x} \cdot \bar{y}_1 \cdot \bar{y}_0$$

$$J_1 = x \cdot \bar{y}_2 \cdot y_0 + \bar{x} \cdot \bar{y}_2 \cdot y_0$$

$$J_0 = 1$$

$$K_2 = x \cdot y_0 + \bar{x} \cdot \bar{y}_1 \cdot \bar{y}_0$$

$$K_1 = x \cdot \bar{y}_2 \cdot y_0 + \bar{x} \cdot \bar{y}_0$$

$$K_0 = 1$$

共10个门。

$y_1 y_0 \backslash xy_2$	0	1	d	d
0	1	d	d	0
1	0	d	d	0
0	0	d	d	1
1	0	d	d	0

$J_2$

$y_1 y_0 \backslash xy_2$	0	1	0	0
0	0	1	0	0
1	0	0	0	1
0	d	d	d	d
1	d	d	d	d

$J_1$

$y_1 y_0 \backslash xy_2$	0	1	1	1
0	1	1	1	1
1	d	d	d	d
0	d	d	d	d
1	1	d	d	1

$J_0$

$y_1 y_0 \backslash xy_2$	0	1	0	d
0	d	1	0	d
1	d	0	1	d
0	d	d	d	d
1	d	d	d	d

$K_2$

$y_1 y_0 \backslash xy_2$	0	d	d	d
0	d	d	d	d
1	d	d	d	d
0	0	d	d	1
1	1	d	d	0

$K_1$


$y_1 y_0 \backslash xy_2$	0	d	d	d
0	d	d	d	d
1	1	1	1	1
0	1	d	d	1
1	d	d	d	d

$K_0$

Q	Q <sup>n+1</sup>	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

激励表

# 六进制可逆计数器逻辑图

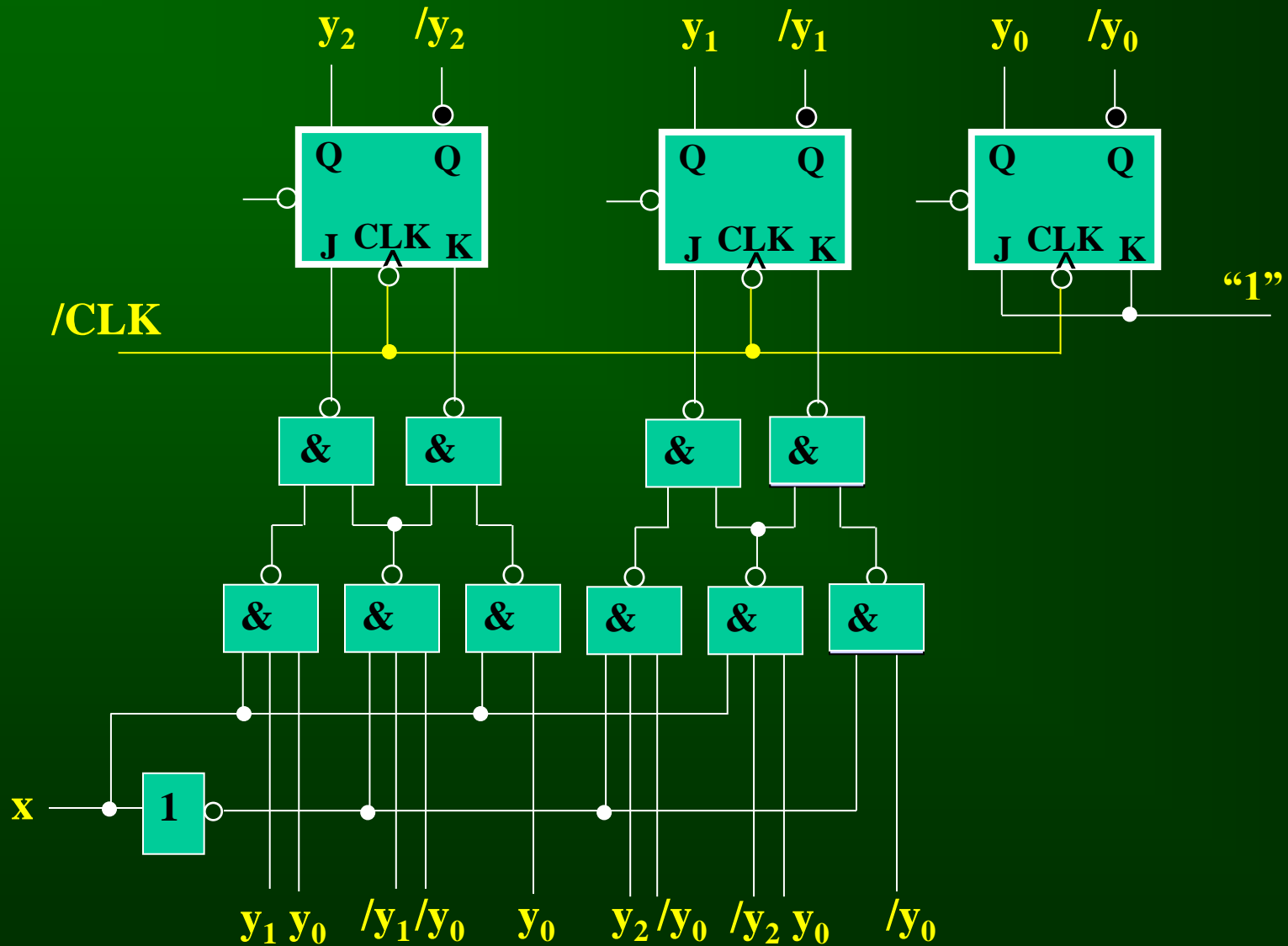

# 电路状态图

$y_2y_1y_0 \backslash x$	0	1
000	101	001
001	000	010
010	001	011
011	010	100
100	011	101
101	100	000
110	101	111
111	110	010

二进制状态表

$xy_2$   
 $y_1y_0$

1	d	d	0
0	d	d	0
0	d	d	1
0	d	d	0

$J_2$

0	1	0	0
0	0	0	1
d	d	d	d
d	d	d	d

$J_1$

1	1	1	1
d	d	d	d
d	d	d	d
1	d	d	1

$J_0$

d	1	0	d
d	0	1	d
d	d	d	d
d	d	d	d


$K_2$

d	d	d	d
d	d	d	d
0	d	d	1
1	d	d	0

$K_1$

d	d	d	d
1	1	1	1
1	d	d	1
d	d	d	d

$K_0$

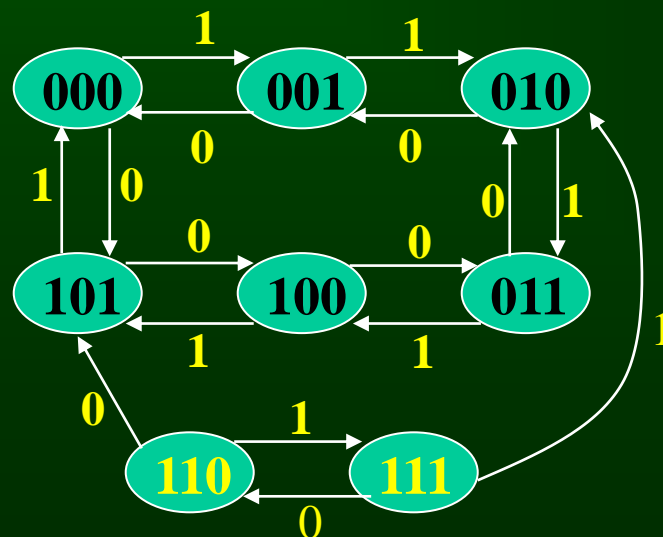



# 另一种激励函数表达式及电路状态图

$$J_2 = x \cdot y_1 \cdot y_0 + \bar{x} \cdot \bar{y}_1 \cdot \bar{y}_0$$

$$K_2 = x \cdot y_0 + \bar{x} \cdot \bar{y}_0$$

$$J_1 = x \cdot \bar{y}_2 \cdot y_0 + \bar{x} \cdot y_2 \cdot \bar{y}_0$$

$$K_1 = K_2$$

$$J_0 = 1 \quad K_0 = 1 \quad \text{共9个门}$$

$xy_2$   
 $y_1y_0$

1	d	d	0
0	d	d	0
0	d	d	1
0	d	d	0

$J_2$

0	1	0	0
0	0	0	1
d	d	d	d
d	d	d	d

$J_1$

1	1	1	1
d	d	d	d
d	d	d	d
1	d	d	1

$J_0$

d	1	0	d
d	0	1	d
d	d	d	d
d	d	d	d

$K_2$


d	d	d	d
d	d	d	d
0	d	d	1
1	d	d	0

$K_1$

d	d	d	d
1	1	1	1
1	d	d	1
d	d	d	d

$K_0$

$y_2y_1y_0 \backslash x$	0	1
000	101	001
001	000	010
010	001	011
011	010	100
100	011	101
101	100	000
110	001	111
111	110	000

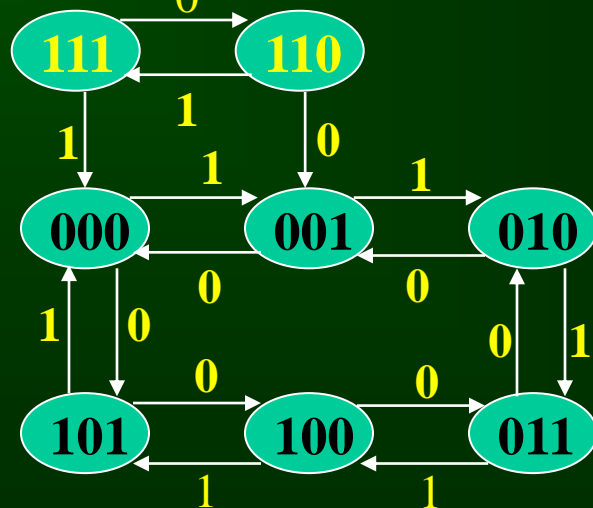

二进制状态表

### 例3 设计八进制步进码计数器。

第一步：列出次态真值表，如右表所示。

$Q_4$	$Q_3$	$Q_2$	$Q_1$	$Q_4^{n+1}$	$Q_3^{n+1}$	$Q_2^{n+1}$	$Q_1^{n+1}$
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	d	d	d	d
0	0	1	1	0	1	1	1
0	1	0	0	d	d	d	d
0	1	0	1	d	d	d	d
0	1	1	0	d	d	d	d
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	d	d	d	d
1	0	1	0	d	d	d	d
1	0	1	1	d	d	d	d
1	1	0	0	1	0	0	0
1	1	0	1	d	d	d	d
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

第二步：根据次态真值表，画出计数器的卡诺图。

$Q_2Q_1$		$Q_4Q_3$	
		00	01
00		d	1
01		d	d
10		1	1
11	d	d	1

$Q_4^{n+1}$

$Q_2Q_1$		$Q_4Q_3$	
		00	01
00		d	
01		d	d
10		1	1
11	d	d	1

$Q_3^{n+1}$

$Q_2Q_1$		$Q_4Q_3$	
		00	01
00		d	
01		1	d
10		1	1
11	d	d	

$Q_2^{n+1}$

$Q_2Q_1$		$Q_4Q_3$	
		00	01
00		1	d
01		1	d
10		1	1
11	d	d	

$Q_1^{n+1}$

次态方程


$$Q_4^{n+1} = Q_3$$

$$Q_3^{n+1} = Q_2$$

$$Q_2^{n+1} = Q_1$$

$$Q_1^{n+1} = \overline{Q_4}$$

电路为单纯的扭环移位寄存器，如图所示：

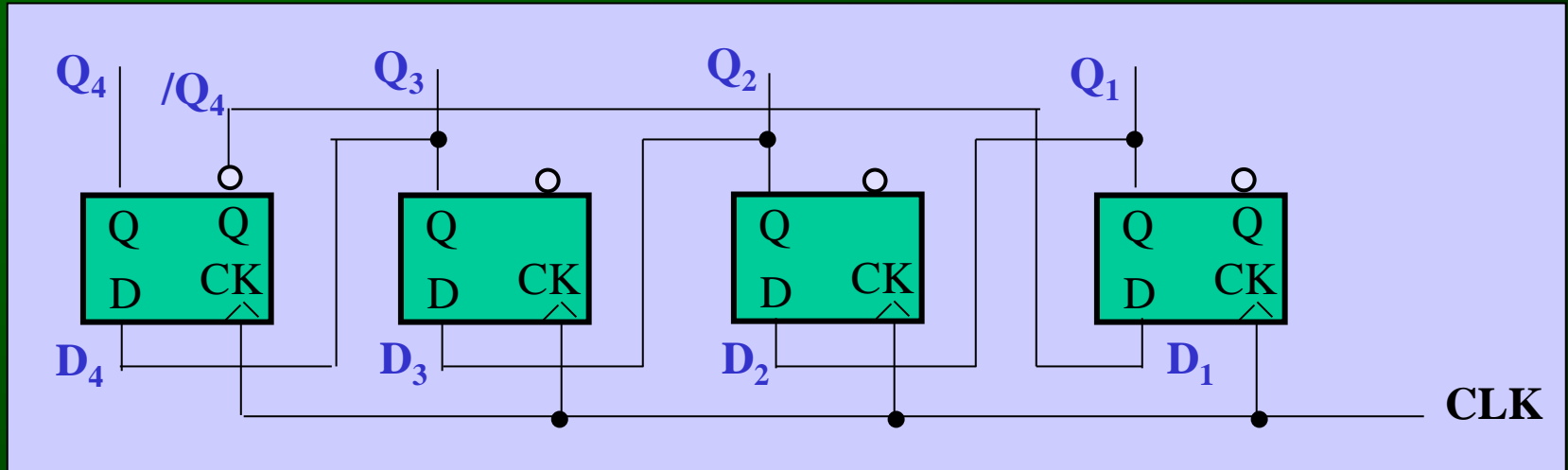


第三步：根据卡诺图确定次态真值表的无关项。


$Q_4Q_3Q_2Q_1$				$Q_4^{n+1}Q_3^{n+1}$ $Q_2^{n+1}Q_1^{n+1}$			
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

## 第四步：分析存在挂起现象的状态表和状态图。

(a) 有效序列

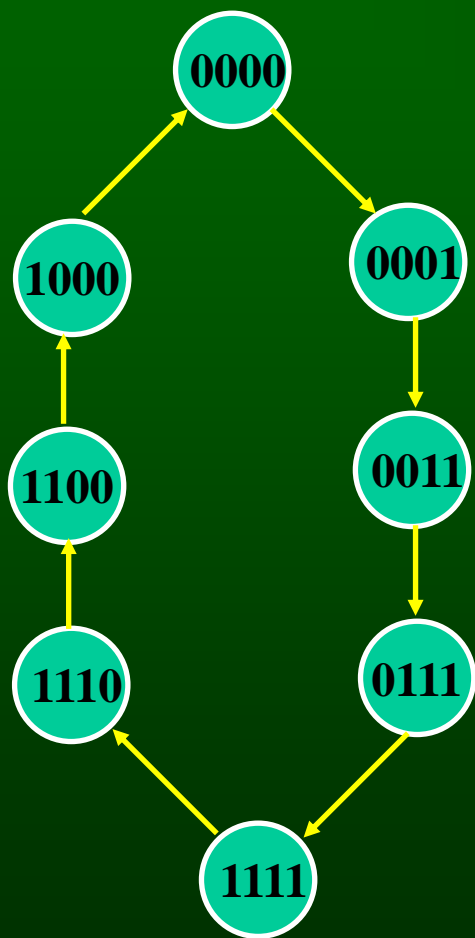

(b) 无效序列

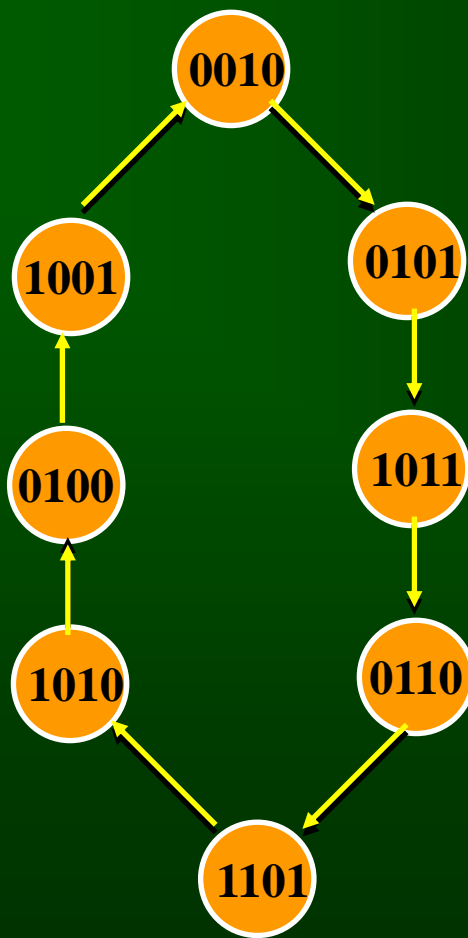

$Q_4 Q_3 Q_2 Q_1$				$Q_4^{n+1} Q_3^{n+1} Q_2^{n+1} Q_1^{n+1}$			
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

# 解决挂起问题

为使电路改动最小，试只改变触发器 $Q_1$ 的输入控制函数 $D_1$ 来解决挂起问题。

$Q_1^{n+1} = D_1$ ，也就是改变 $Q_1^{n+1}$ 卡诺图中无关项的取舍。可改变的只是 $Q_1$ 输入端的原无关项部分，而且并不是改变每个无关项都能完全解决“挂起”问题。

注意：能解决挂起问题的是“\*”的部分。

当然，并不要求把所有打“\*”的部分改变，那么应当改哪些最好？应根据卡诺图来判断。

$m_4$

$m_6$

$m_9$

$m_{11}$

$Q_4Q_3Q_2Q_1$				$Q_4^{n+1}Q_3^{n+1}$ $Q_2^{n+1}Q_1^{n+1}$			
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

修改 $Q_1$ 的输入来解决挂起问题。

方案1（蓝色）： $Q_1^{n+1} = \overline{Q_4} \overline{Q_3} + \overline{Q_4} Q_1$

这就是**Johnson**计数器的设计方案。

$Q_4 Q_3$  /  $Q_2 Q_1$

1	*d		
1	d	d	d
1	1		d
d	*d		d

$Q_1^{n+1}$

$m_4$

$m_6$

$m_9$

$m_{11}$


$Q_4 Q_3 Q_2 Q_1$				$Q_4^{n+1} Q_3^{n+1} Q_2^{n+1} Q_1^{n+1}$			
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0




修改 $Q_1$ 的输入来解决挂起问题。

**方案1**（蓝色）： $Q_1^{n+1} = \overline{Q_4} \overline{Q_3} + \overline{Q_4} Q_1$

这就是**Johnson** 计数器的设计方案。

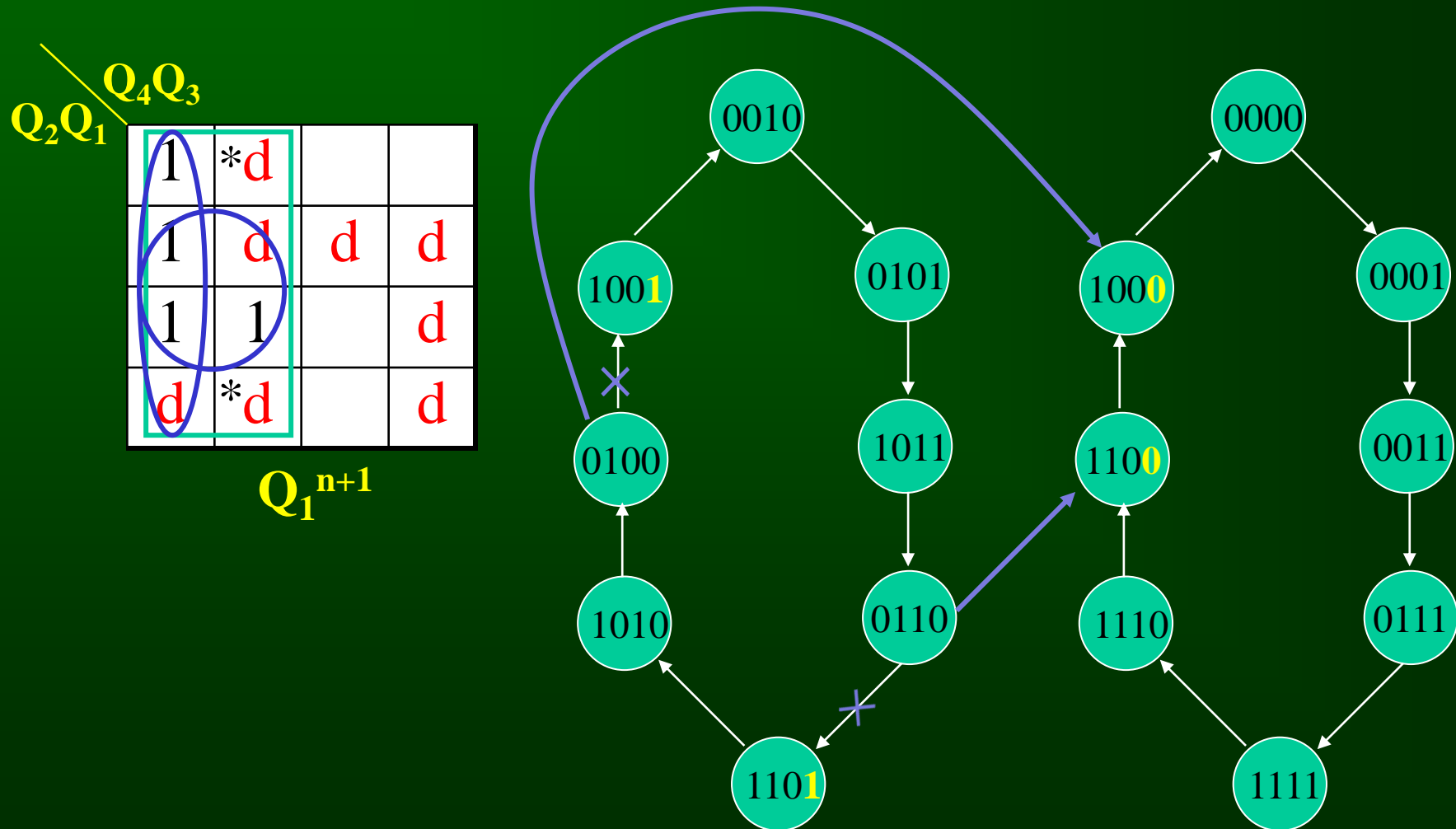

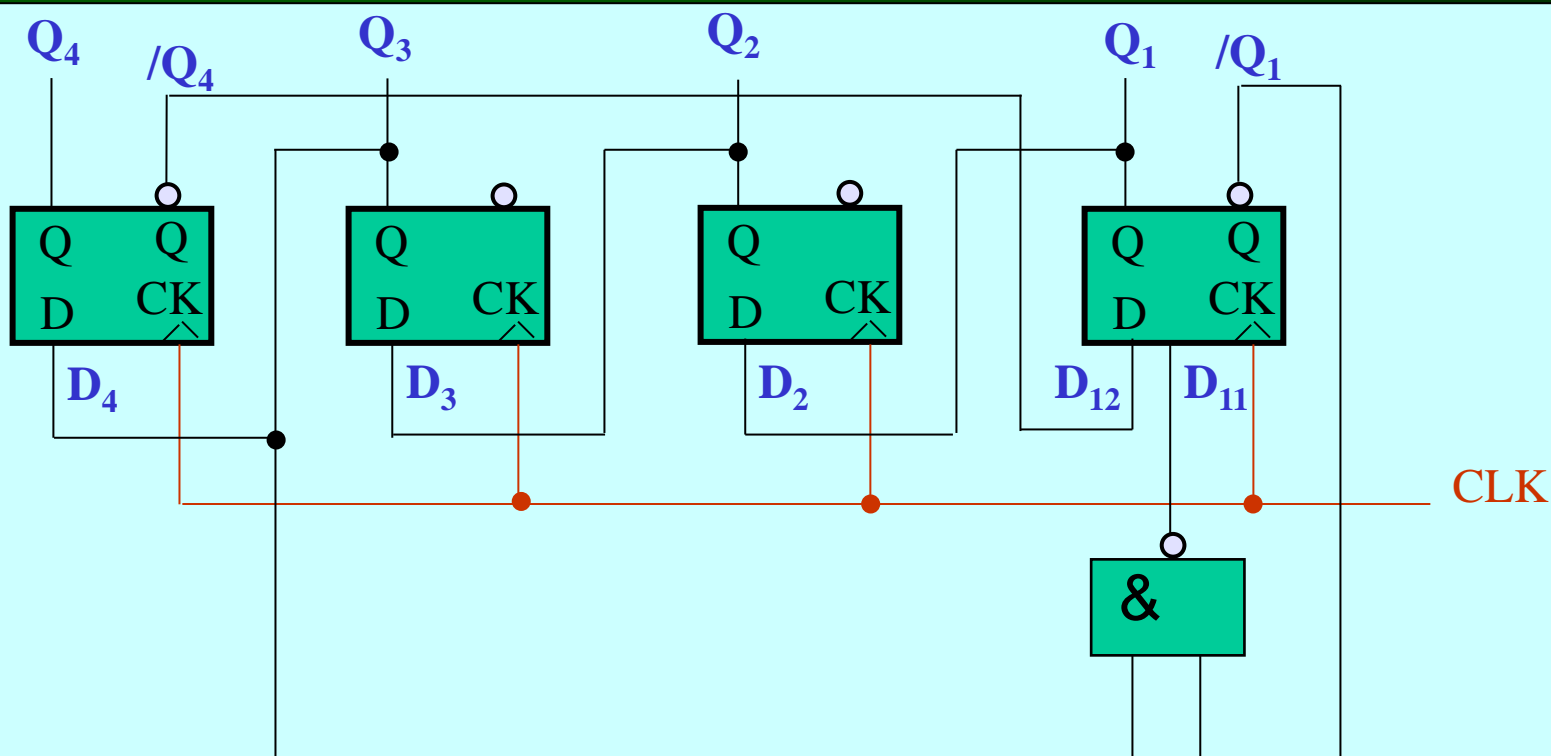该电路共有16个状态。只要电路的初始态为状态图闭环中某一状态，在时钟脉冲作用下，电路将按箭头所指方向在闭环环中8个状态间循环。这是一个模8步进码计数器。时钟脉冲就是计数信号，这8个状态称为“有效序列”。在闭环以外的8个状态称为“无效序列”。这种电路称为格雷码计数器或 Johnson 计数器，也叫“自恢复扭环移位寄存器”。



修改 $Q_1$ 的输入来解决挂起问题。

方案2（紫色）： $Q_1^{n+1} = \bar{Q}_4 + \bar{Q}_3 Q_1$

1	d		
1	d	d	d*
1	1		d*
d	d		d

$Q_1^{n+1}$

$m_4$

$m_6$

$m_9$


$m_{11}$

$Q_4 Q_3 Q_2 Q_1$	$Q_4^{n+1} Q_3^{n+1} Q_2^{n+1} Q_1^{n+1}$
0 0 0 0	0 0 0 1
0 0 0 1	0 0 1 1
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 1
0 1 0 0	1 0 0 1 *
0 1 0 1	1 0 1 1
0 1 1 0	1 1 0 1 *
0 1 1 1	1 1 1 1
1 0 0 0	0 0 0 0
1 0 0 1	0 0 1 0 *
1 0 1 0	0 1 0 0
1 0 1 1	0 1 1 0 *
1 1 0 0	1 0 0 0
1 1 0 1	1 0 1 0
1 1 1 0	1 1 0 0
1 1 1 1	1 1 1 0

修改 $Q_1$ 的输入来解决挂起问题。

**方案2（紫色）：**  $Q_1^{n+1} = \overline{Q_4} + \overline{Q_3} Q_1$

Diagram illustrating a 2D lattice structure with a 4x4 grid. The grid is labeled with  $Q_2Q_1$  on the left and  $Q_4Q_3$  on the top. The bottom is labeled  $Q_1^{n+1}$ . The grid contains black and red numbers and letters. A purple box highlights a 2x2 subgrid of black numbers (1, 1, 1, 1). A red box highlights a 2x2 subgrid of red letters (d, d, d, d). A red box highlights a 2x2 subgrid of red letters (d, d, d, d). A red box highlights a 2x2 subgrid of red letters (d, d, d, d).

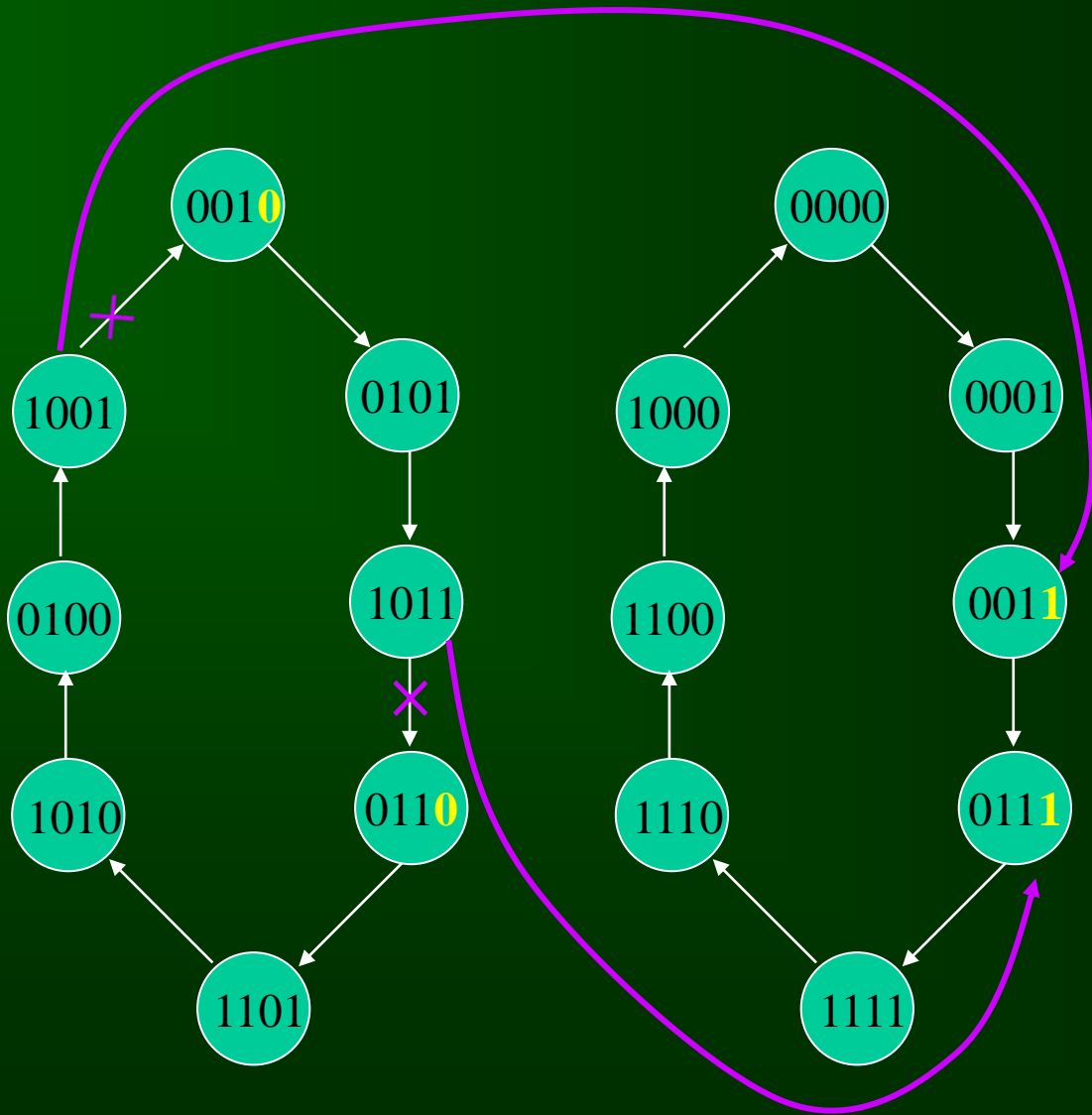

修改 $Q_2$ 的输入来解决挂起问题。

方案1（蓝色）：

$Q_4Q_3$  /  $Q_2Q_1$

	d		
1	d	*d	*d
1	1	1	d
d	d		d

$Q_2^{n+1}$

$$Q_2^{n+1} = \overline{Q_4} Q_1 + Q_2 Q_1$$

$m_2$

$m_6$

$m_9$

$m_{13}$

$Q_4Q_3Q_2Q_1$				$Q_4^{n+1}Q_3^{n+1}$ $Q_2^{n+1}Q_1^{n+1}$			
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	* 1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	* 1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	* 0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	* 0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0


修改 $Q_2$ 的输入来解决挂起问题。

方案1（蓝色）： $Q_2^{n+1} = \overline{Q_4} Q_1 + Q_2 Q_1$

$Q_4 Q_3$  /  $Q_2 Q_1$

	d		
1	d	*d	*d
1	1	1	d
d	d		d

$Q_2^{n+1}$

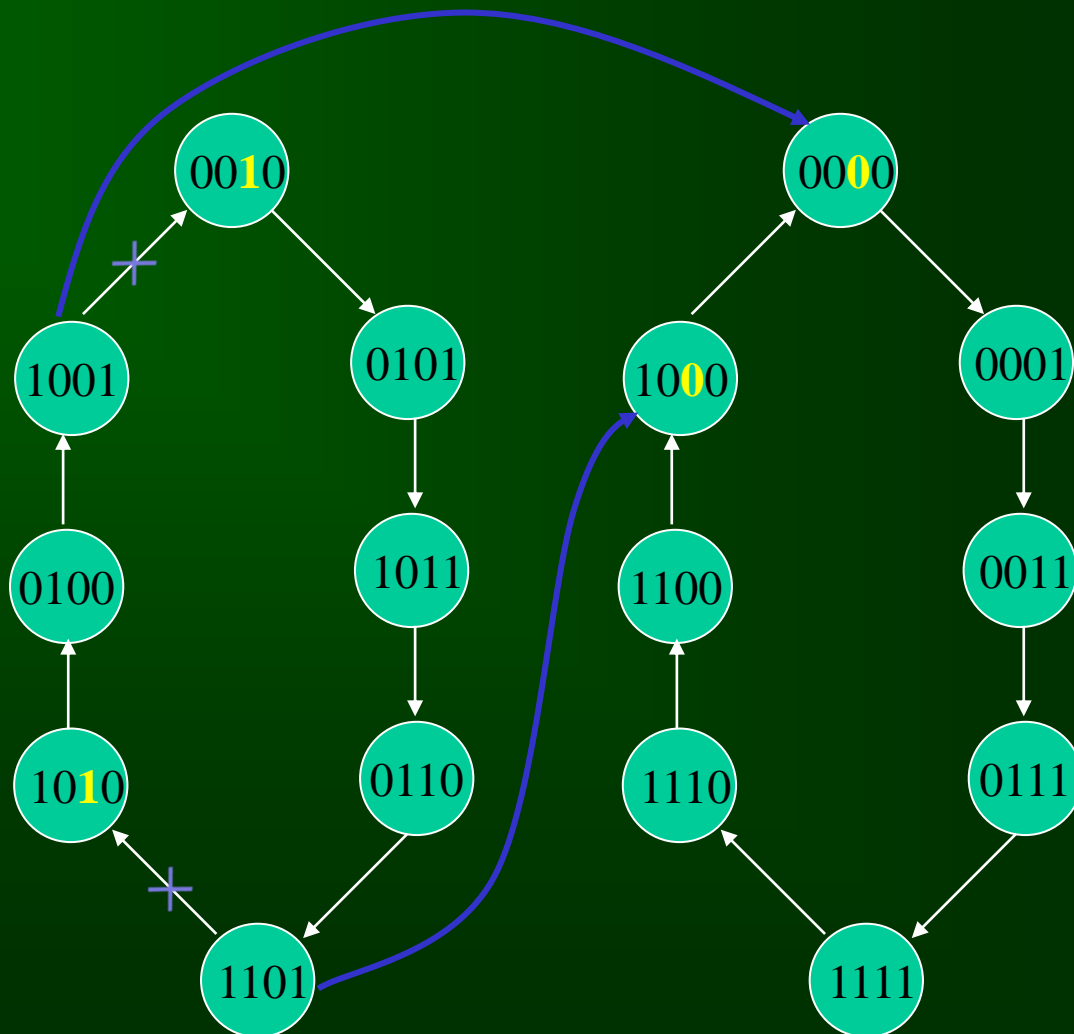

修改 $Q_2$ 的输入来解决挂起问题。

方案2（紫色）： $Q_2^{n+1} = Q_1 + \bar{Q}_4 Q_2$

$Q_2 Q_1 \backslash Q_4 Q_3$

	d		
1	d	d	d
1	1	1	d
*d	*d		d

$Q_2^{n+1}$

$m_2$

$m_6$

$m_9$

$m_{13}$

$Q_4 Q_3 Q_2 Q_1$

$Q_4^{n+1} Q_3^{n+1}$

$Q_2^{n+1} Q_1^{n+1}$

0 0 0 0

0 0 0 1

0 0 1 0

0 0 1 1

0 1 0 0

0 1 0 1

0 1 1 0

0 1 1 1

1 0 0 0

1 0 0 1

1 0 1 0

1 0 1 1

1 1 0 0

1 1 0 1

1 1 1 0

1 1 1 1

0 0 0 1

0 0 1 1

0 1 0 \*

0 1 1 1

1 0 0 1

1 0 1 1

1 1 0 \*

1 1 1 1

0 0 0 0

0 0 1 \*

0 1 0 0

0 1 1 0

1 0 0 0

1 0 1 \*

1 1 0 0

1 1 1 0


修改 $Q_2$ 的输入来解决挂起问题。

方案2（紫色）： $Q_2^{n+1} = Q_1 + \bar{Q}_4 Q_2$

$Q_2 Q_1 \backslash Q_4 Q_3$

	d		
1	d	d	d
1	1	1	d
*d	*d		d

$Q_2^{n+1}$

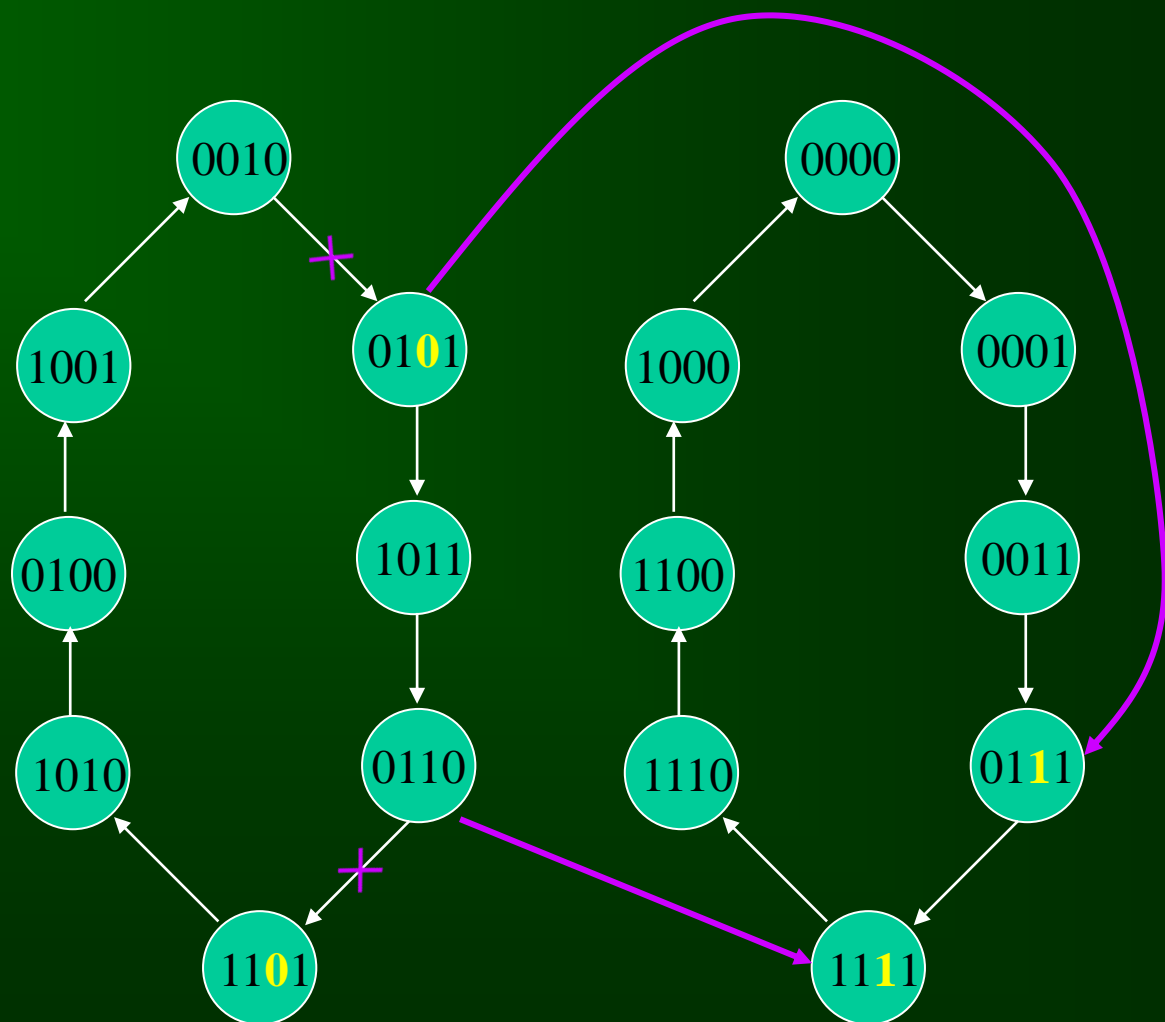



**例4** 用D触发器设计一个4位自校正环形计数器，其状态位： $1110 \rightarrow 1101 \rightarrow 1011 \rightarrow 0111 \rightarrow 1110$ 。（书例3-11）

解：根据题意，得到如下二进制状态表，即可得到：

$$Q_3^{n+1}=Q_2, \quad Q_2^{n+1}=Q_1, \\ Q_1^{n+1}=Q_0, \quad Q_0^{n+1}=Q_3。$$

则有

$$D_3=Q_2, \quad D_2=Q_1, \\ D_1=Q_0, \quad D_0=Q_3。$$

电路如下下页所示。

$m_{14}$

$m_{13}$

$m_{11}$

$m_7$

$Q_3Q_2Q_1Q_0$	$Q_3^{n+1}Q_2^{n+1}Q_1^{n+1}Q_0^{n+1}$
0000	<i>d d d d</i>
0001	<i>d d d d</i>
0010	<i>d d d d</i>
0011	<i>d d d d</i>
0100	<i>d d d d</i>
0101	<i>d d d d</i>
0110	<i>d d d d</i>
1000	<i>d d d d</i>
1001	<i>d d d d</i>
1010	<i>d d d d</i>
1100	<i>d d d d</i>
1111	<i>d d d d</i>
<b>1110</b>	<b>1 1 0 1</b>
<b>1101</b>	<b>1 0 1 1</b>
<b>1011</b>	<b>0 1 1 1</b>
<b>0111</b>	<b>1 1 1 0</b>

表（a） 二进制状态表

# 练习

$Q_1Q_0 \backslash Q_3Q_2$		00	01	10	11
00	d	d	d	d	d
01	d	d	1	d	d
10	d	1	d	d	d
11	d	d	1	d	d

$Q_3^{n+1}$

$Q_1Q_0 \backslash Q_3Q_2$		00	01	10	11
00	d	d	d	d	d
01	d	d	d	d	d
10	d	1	d	1	d
11	d	d	1	d	d

$Q_2^{n+1}$

$Q_1Q_0 \backslash Q_3Q_2$		00	01	10	11
00	d	d	d	d	d
01	d	d	1	d	d
10	d	1	d	1	d
11	d	d	d	d	d

$Q_1^{n+1}$

$Q_1Q_0 \backslash Q_3Q_2$		00	01	10	11
00	d	d	d	d	d
01	d	d	1	d	d
10	d	d	d	1	d
11	d	d	1	d	d


$Q_0^{n+1}$

$$Q_3^{n+1} = Q_2,$$

$$Q_2^{n+1} = Q_1,$$


$$Q_1^{n+1} = Q_0,$$

$$Q_0^{n+1} = Q_3.$$

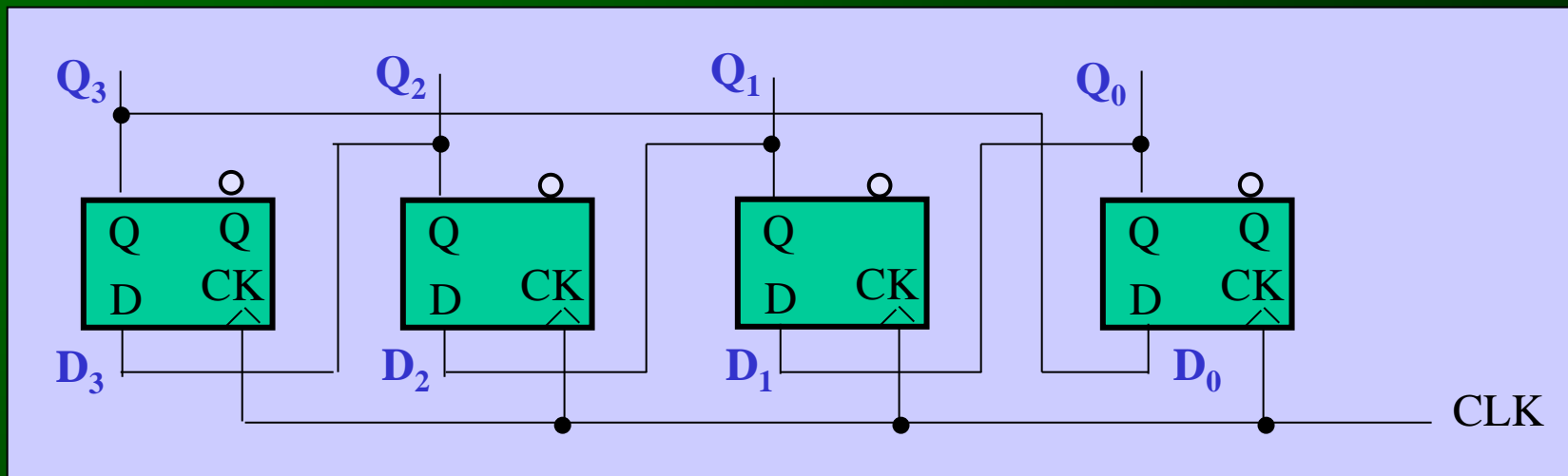

分析并发现：电路可能停在0000或1111，  
或在0001→0010→0100→1000→0001中循环，  
或在0011→0110→1100→1001→0011中循环，  
或在0101→1010→0101中循环，  
即停留在无效状态或在无效状态中循环。也就是存在“挂起现象”：


# 练习

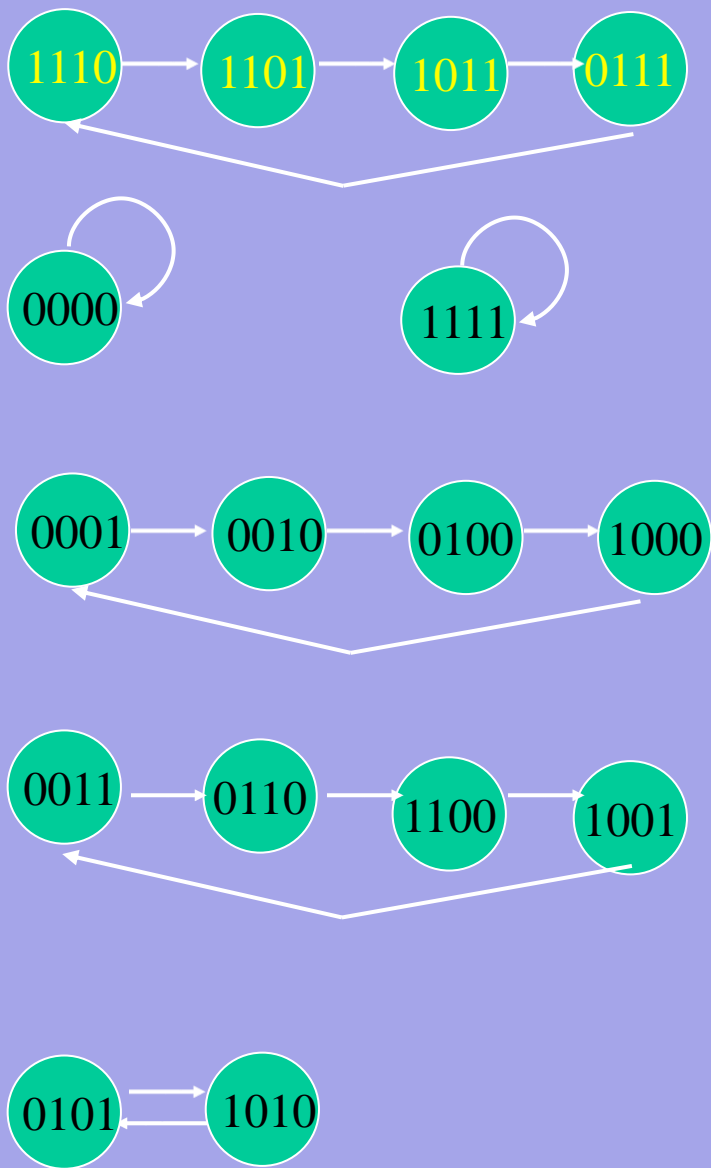

	$Q_3 Q_2 Q_1 Q_0$	$Q_3^{n+1} Q_2^{n+1} Q_1^{n+1} Q_0^{n+1}$
$m_0$	0000	0 0 0 0
$m_1$	0001	0 0 1 0
$m_2$	0010	0 1 0 0
$m_3$	0011	0 1 1 0
$m_4$	0100	1 0 0 0
$m_5$	0101	1 0 1 0
$m_6$	0110	1 1 0 0
	1000	0 0 0 1
	1001	0 0 1 1
	1010	0 1 0 1
	1100	1 0 0 1
$m_{15}$	1111	1 1 1 1
$m_{14}$	1110	1 1 0 1
$m_{13}$	1101	1 0 1 1
$m_{11}$	1011	0 1 1 1
$m_7$	0111	1 1 1 0

表 (b) 挂起的二进制状态表

# 练习

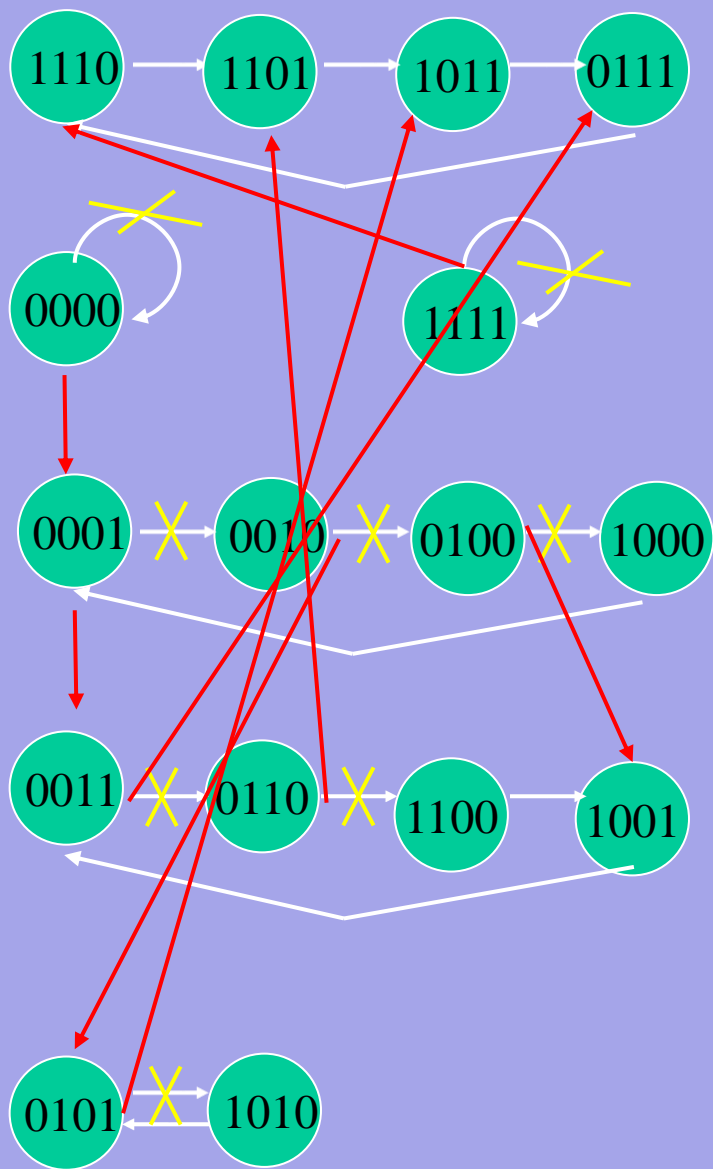

	$Q_3Q_2Q_1Q_0$	$Q_3^{n+1}Q_2^{n+1}Q_1^{n+1}Q_0^{n+1}$
$m_0$	0000	0 0 0 1
$m_1$	0001	0 0 1 1
$m_2$	0010	0 1 0 1
$m_3$	0011	0 1 1 1
$m_4$	0100	1 0 0 1
$m_5$	0101	1 0 1 1
$m_6$	0110	1 1 0 1
	1000	0 0 0 1
	1001	0 0 1 1
	1010	0 1 0 1
	1100	1 0 0 1
$m_{15}$	1111	1 1 1 0
$m_{14}$	1110	1 1 0 1
$m_{13}$	1101	1 0 1 1
$m_{11}$	1011	0 1 1 1
$m_7$	0111	1 1 1 0

表 (c) 消除挂起的二进制状态表

$Q_3 Q_2 Q_1 Q_0$	$Q_3^{n+1} Q_2^{n+1} Q_1^{n+1} Q_0^{n+1}$
0000	0 0 0 1
0001	0 0 1 1
0010	0 1 0 1
0011	0 1 1 1
0100	1 0 0 1
0101	1 0 1 1
0110	1 1 0 1
1000	0 0 0 1
1001	0 0 1 1
1010	0 1 0 1
1100	1 0 0 1
1111	1 1 1 0
1110	1 1 0 1
1101	1 0 1 1
1011	0 1 1 1
0111	1 1 1 0

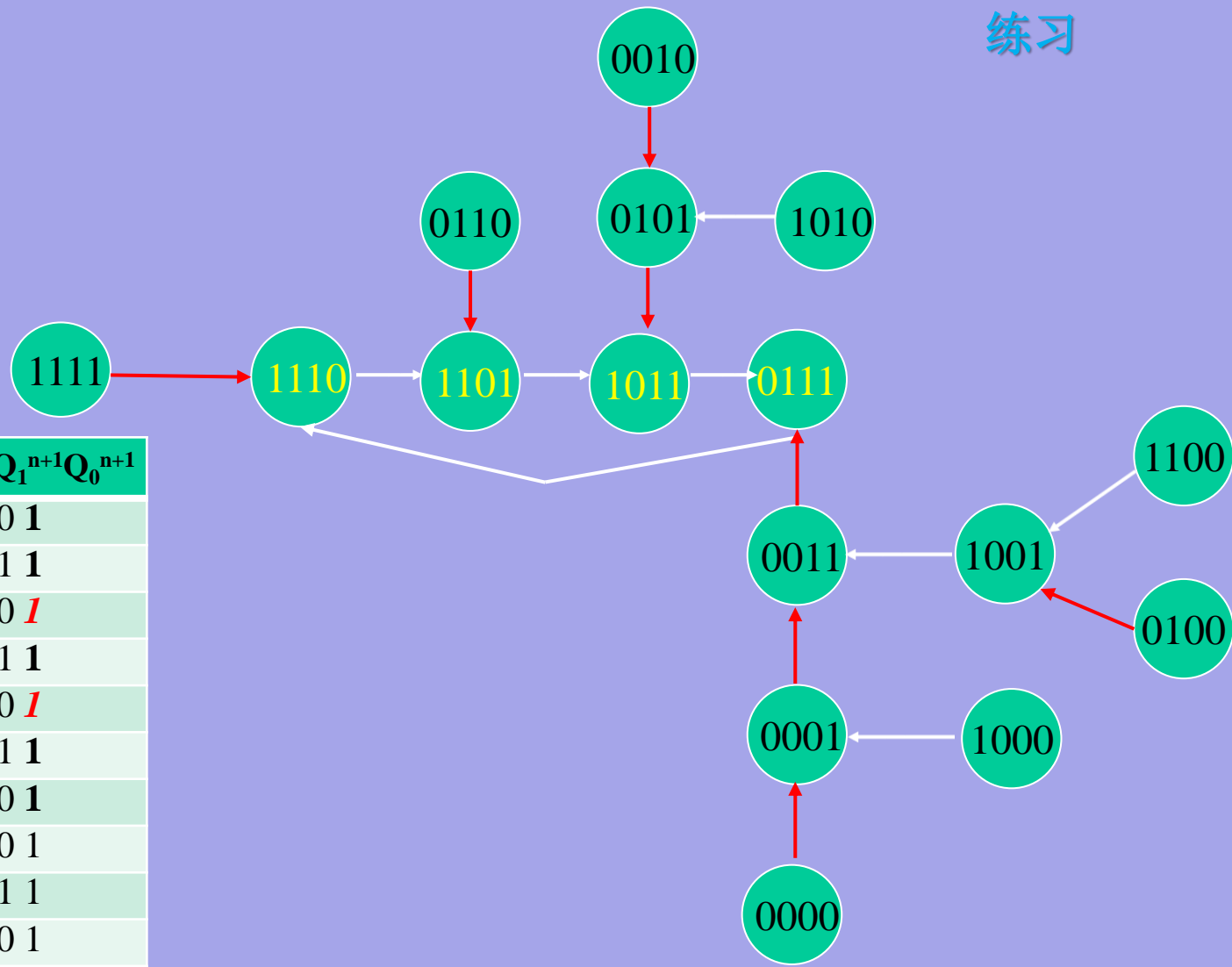


表 (c) 消除挂起的二进制状态表

$Q_3Q_2$   
 $Q_1Q_0$

1	1	1	1
1	1	1	1
1			1
1	1	1	1

$Q_0^{n+1} = \overline{Q_2} + \overline{Q_1} + \overline{Q_0}$

练习

$Q_3Q_2$   
 $Q_1Q_0$

d	d	d	d
d	d	1	d
d	d	d	1
d	d	1	d

$Q_0^{n+1} = Q_3$

$Q_3Q_2$   
 $Q_1Q_0$


1		1	1
1	1	1	1
1			1
	1	1	1

$Q_0^{n+1}$


	$Q_3Q_2Q_1Q_0$	$Q_3^{n+1}Q_2^{n+1}Q_1^{n+1}Q_0^{n+1}$
$m_0$	0000	0 0 0 1
$m_1$	0001	0 0 1 1
$m_2$	0010	0 1 0 1
$m_3$	0011	0 1 1 1
$m_4$	0100	1 0 0 1
$m_5$	0101	1 0 1 1
$m_6$	0110	1 1 0 1
	1000	0 0 0 1
	1001	0 0 1 1
	1010	0 1 0 1
	1100	1 0 0 1
$m_{15}$	1111	1 1 1 0
$m_{14}$	1110	1 1 0 1
$m_{13}$	1101	1 0 1 1
$m_{11}$	1011	0 1 1 1
$m_7$	0111	1 1 1 0

表 (c) 消除挂起的二进制状态表

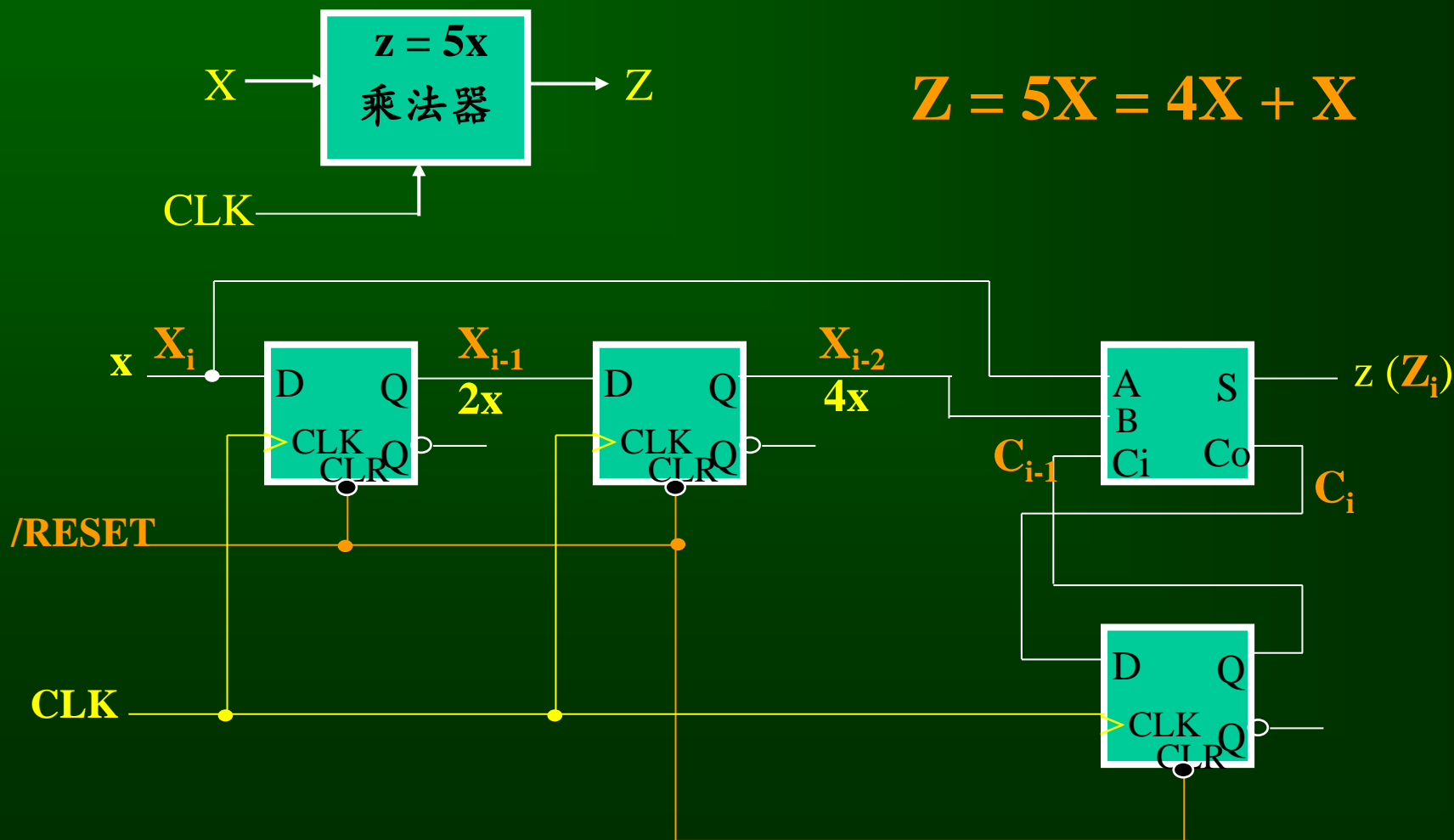**例5** 设计一个 **n 位二进制串行乘法器**，该乘法器有一个**输入端 X** 及一个**输出端 Z**，输入 X 为由低位开始的二进制串行序列信号，输出 Z 为另一个串行序列(由低位开始输出)，且  **$Z = 5X$** 。(书例3-10)





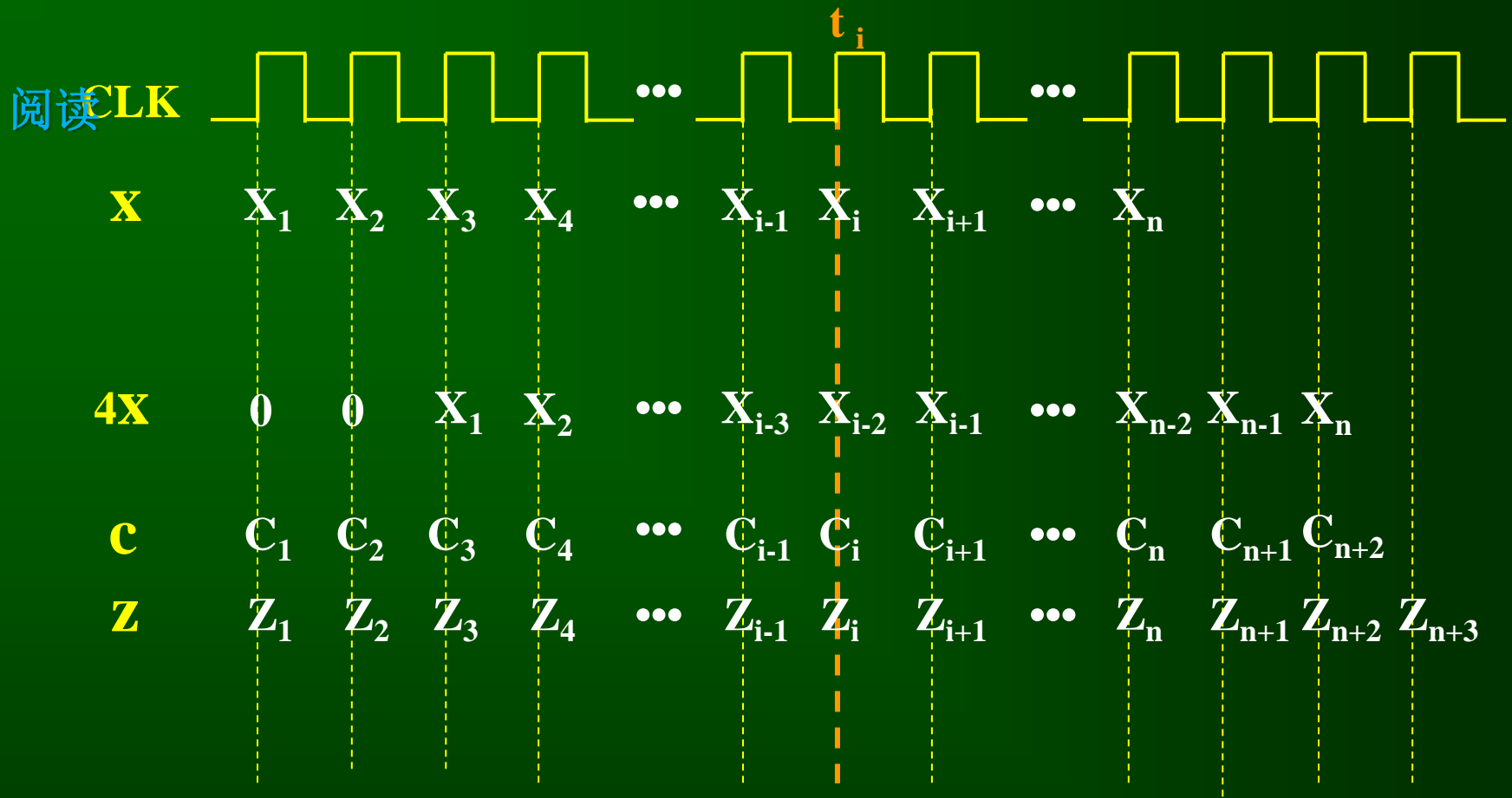

$$Z_i = X_i \oplus X_{i-2} \oplus C_{i-1}$$

$$C_i = X_i X_{i-2} + X_i C_{i-1} + X_{i-2} C_{i-1}$$

其中:  $X_i$  为  $t_i$  时刻的输入信号,

$X_{i-2}$  为  $t_i$  时刻前两个节拍的输入信号,


$C_{i-1}$  为  $t_i$  时刻前一个节拍的加法进位信号。



$$S_i = A \oplus B \oplus C_{i-1}$$

$$C_i = AB + AC_{i-1} + BC_{i-1}$$

阅读

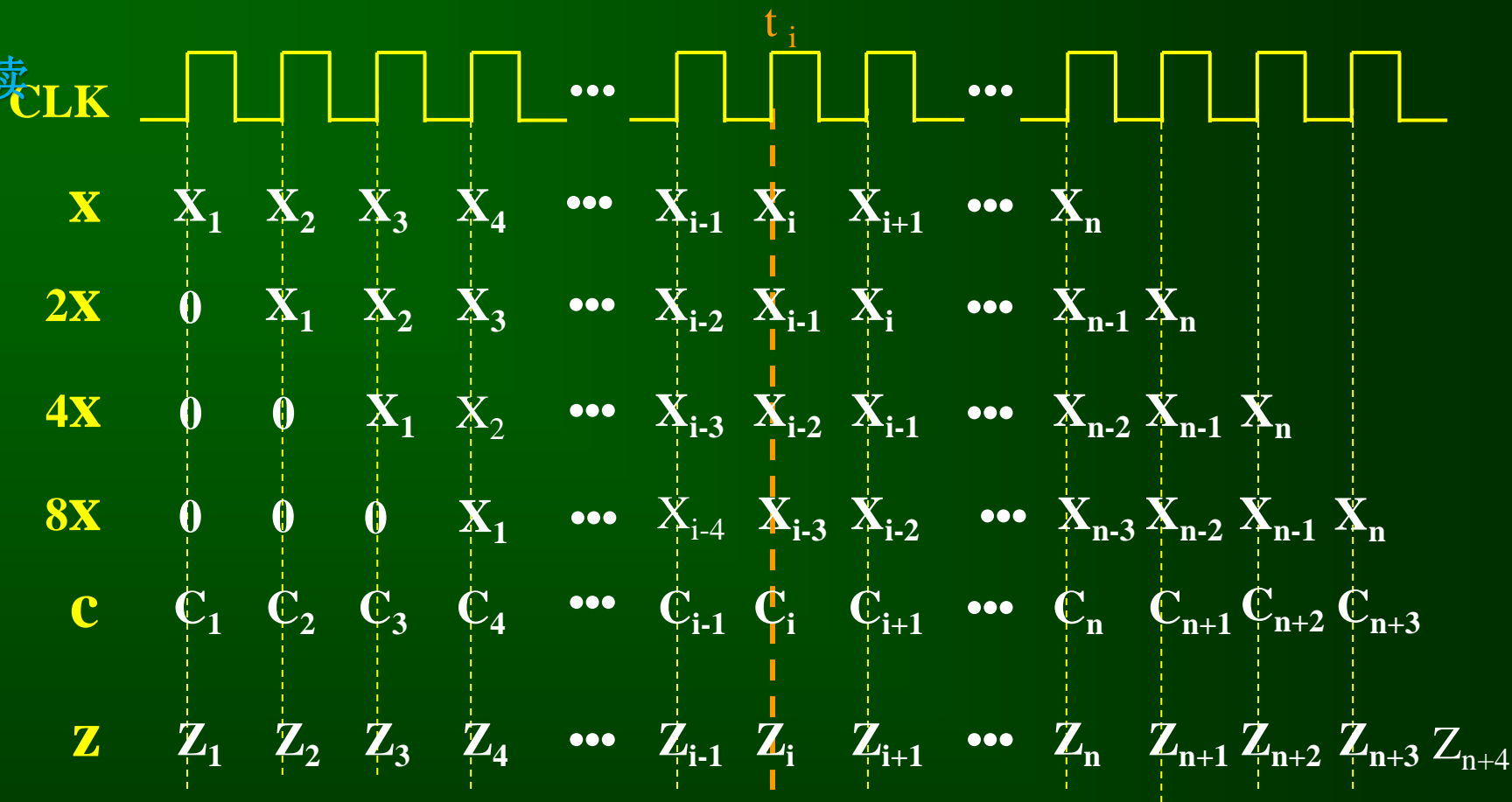

$z = kx$ 。其中  $k$  为控制端信号  $K_3 K_2 K_1 K_0$  所构成的二进制代码数值 ( $0 \leq k \leq 15$ )。

$$Z_i \rightarrow K_3 x_{i-3} \oplus K_2 x_{i-2} \oplus K_1 x_{i-1} \oplus K_0 x_i$$